



# higher education & training

Department:  
Higher Education and Training  
**REPUBLIC OF SOUTH AFRICA**


## NATIONAL CERTIFICATE ELECTROTECHNICS N4

(8080074)

**21 November 2023 (X-paper)  
09:00–12:00**

**Calculators may be used.**

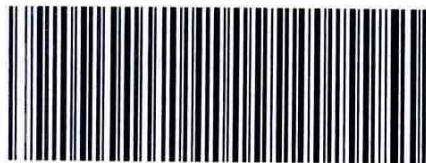**This question paper consists of 7 pages and a formula sheet of 3 pages.**



020Q1E2321005940

03036769

=====  
020Q1E2321  
=====



## QUESTION 1: PRINCIPLES OF ELECTRICITY

- 1.1 Choose a term from COLUMN B that matches a description in COLUMN A. Write only the letter (A–K) next to the question number (1.1.1–1.1.10) in the ANSWER BOOK.

	COLUMN A	COLUMN B
1.1.1	An atom that has lost or gained one or more electrons	A Norton's theorem
1.1.2	The force that tends to produce an electric current in a circuit	B negative temperature coefficient of resistance
1.1.3	When an increase in the temperature of a material causes the resistance of the material to fall	C capacitance
1.1.4	When an increase in the temperature of a material causes the resistance of the material to rise	D like poles repel each other
1.1.5	Any network that has two terminals and consists of resistances, voltage sources and current sources can be replaced by a single current source in parallel with a single resistance	E ion
1.1.6	When a conductor moves through a coil, a voltage is induced in it, causing the current to flow	F Lenz's law
1.1.7	When two magnets are placed close to each other	G permeability
1.1.8	The direction of induced EMF is such that the current it sets up is in the opposite direction	H electromotive force
1.1.9	The ease with which a magnetic field can be established in a material compared to the ease with which the same magnetic field can be established in air	I Faraday's law
1.1.10	The ratio between the charge and the applied voltage	J electromagnetic induction
		K positive temperature coefficient of resistance

(10 × 1)

(10)



- 1.2 An aluminium wire 7,5 m long is connected in parallel with a copper wire that is 6 m long. When a current of 5 A is passed through the combination, it is found that the current through the aluminium wire is 3 A. The diameter of the aluminium wire is 1 mm.

Determine the diameter of the copper wire. The resistivity of copper is 0,0017 micro-ohm metres and that of aluminium 0,028 micro-ohm metres. (10)

- 1.3 Apply Kirchhoff's law to FIGURE 1 below, and determine the value of the current in each branch of the circuit.

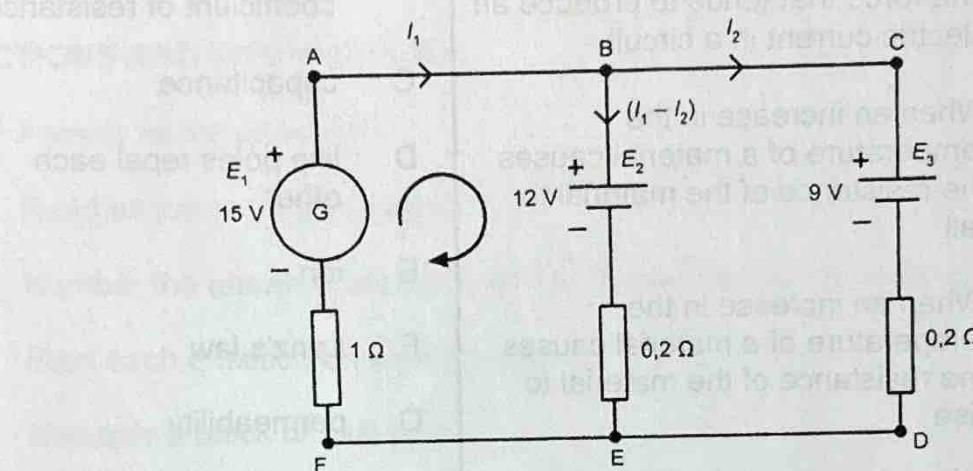


FIGURE 1

(10)  
[30]

## QUESTION 2: DC MACHINES

- 2.1 FIGURE 2 below shows the construction of a DC machine. Give the correct name for each of the labelled parts (A–H).

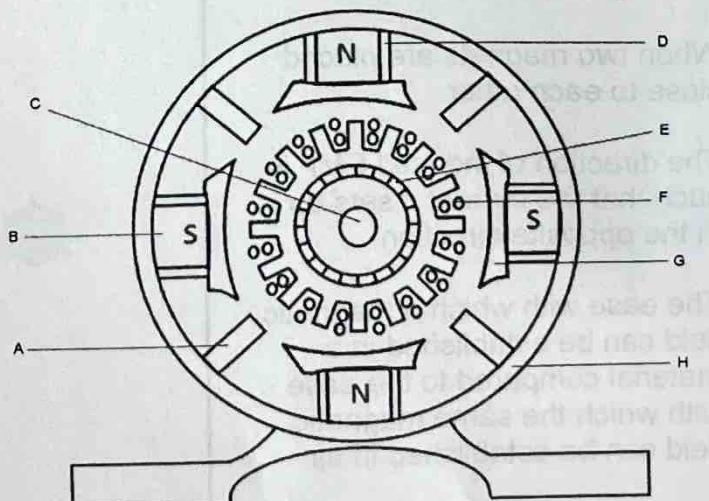


FIGURE 2

(8)



2.2

The open-circuit characteristic of a DC shunt generator, running at 600 r/m, is:

Current (A)	1	2	3	4	5	6	7	8	9	10
EMF (V)	100	260	390	470	530	570	600	620	630	640

Determine the voltage to which the machine will build up if:

- 2.2.1 The speed is 600 r/min and the resistance of the field circuit is  $84 \Omega$  (6)

- 2.2.2 The speed is increased to 660 r/min and the resistance of the field circuit is reduced to  $72 \Omega$  (6) [20]

### QUESTION 3: AC THEORY

- 3.1 The armature of an alternator rotates at 3 000 rev/min between the poles of a magnet. The maximum voltage of the generated wave is 35,36 V and the waveform is sinusoidal.

Calculate the following:

- 3.1.1 The frequency (1)

- 3.1.2 The instantaneous EMF after 0,004 seconds (2)

- 3.1.3 The time taken from the instant zero to reach 20 V for the first time (5)

- 3.2 Define the term *phasor diagram*. (2)

- 3.3 A coil with a resistance of  $20 \Omega$  and an inductance of  $51 \text{ mH}$  is connected in series with a  $318\text{-}\mu\text{F}$  capacitor. This circuit is connected across a 220-V, 50-Hz supply. (1) [20]

Calculate the following:

- 3.3.1 The inductive and capacitive reactance of the circuit (2)


- 3.3.2 The voltage drop across the coil (7)

- 3.3.3 The voltage drop across the capacitor (1) [20]



## QUESTION 4: TRANSFORMERS

- 4.1 A transformer working on no load draws 2,5 A from the supply at a power factor of 0,3 lagging. Calculate the following:
- The no-load phase angle (1)
  - The magnetising component of  $I_0$  (2)
  - The core loss component of  $I_0$  (2)
- 4.2 FIGURE 3 below shows an oil-immersed air-cooled transformer. Name the FIVE parts (A–E).

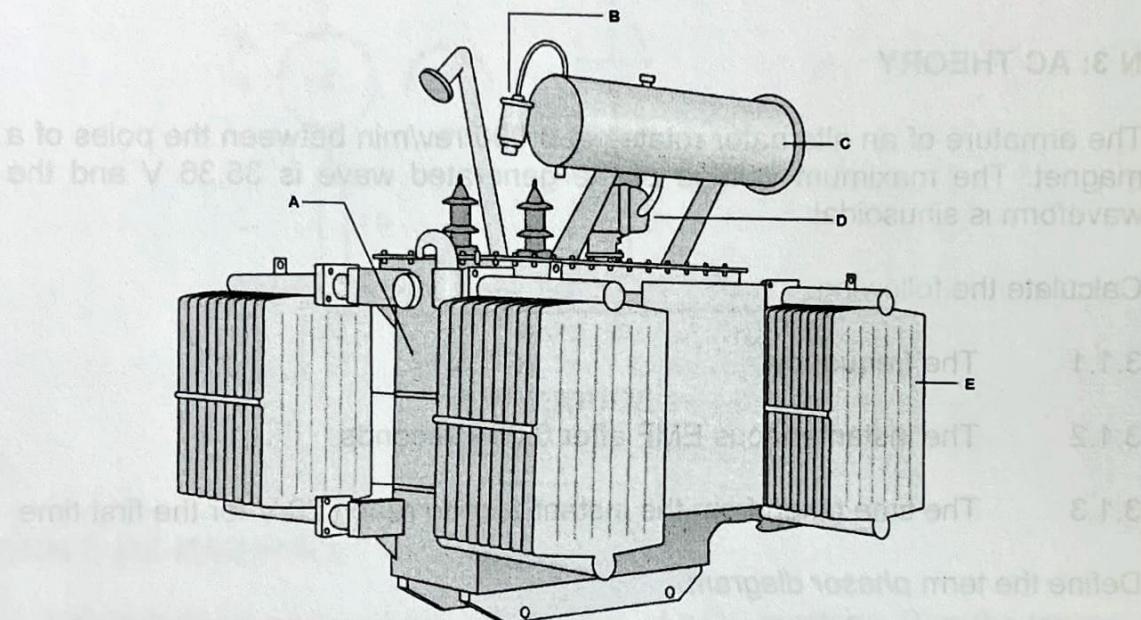

**FIGURE 3**

(5)  
[10]

## QUESTION 5: AC MACHINES

- 5.1 Draw a fully labelled circuit diagram of a capacitor-start, capacitor-run single-phase induction motor. (5)
- 5.2 Name TWO disadvantages of a single-phase induction motor over a three-phase induction motor. (2)
- 5.3 Briefly explain how to reverse the direction of rotation of a single-phase, split-phase induction motor. (3)  
[10]



**QUESTION 6: GENERATION AND SUPPLY OF AC POWER AND MEASURING INSTRUMENTS**

- 6.1 Power stations derive their names from the method used to drive their turbines.  
Name THREE types of power stations that do not rely on a vast quantity of water to operate.

(3)

- 6.2 State TWO reasons for stepping up the voltage on transmission lines. (2)

- 6.3 Complete the following sentence by writing only the missing word or words next to the question number (6.3) in the ANSWER BOOK.

In order to connect a ... in a circuit by means of a shunt resistor and multiplier, the current coil is connected across a shunt resistor and the voltage coil in series with a multiplier.



(1)

- 6.4 A moving-coil instrument has a resistance of  $30\ \Omega$  and gives a full-scale deflection when 50 mA flows through it. Calculate the value of the additional circuit component required to enable the instrument to be used as:

6.4.1 An ammeter, reading 0–5 A



6.4.2 A voltmeter, reading 0–50 V

(2  $\times$  2)

(4)

[10]

**TOTAL: 100**



**ELECTROTECHNICS N4****FORMULA SHEET**

Any applicable formula may also be used.

**PRINCIPLES OF ELECTRICITY**

1.  $E = V + Ir$

2.  $V = IR$

3.  $R_T = R_{se} = R_1 + R_2 + R_3 + \dots + R_n$

4.  $\frac{1}{R_T} = \frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_n}$

5.  $P = VI = I^2R = \frac{V^2}{R}$

6.  $\eta = \frac{P_o}{P_{in}} \times 100$

7.  $R = \rho \frac{l}{A}$

8.  $A = \frac{\pi d^2}{4}$

9.  $\frac{R_1}{R_2} = \frac{1 + \alpha_0 T_1}{1 + \alpha_0 T_2}$

10.  $R_t = R_\theta [1 + \alpha_\theta (t - \theta)]$

11.  $R_T = R_1 + \frac{R_2 \times R_3}{R_2 + R_3}$

12.  $I_{SC} = I_N = \left[ \frac{R_2}{R_2 + R_3} \right] I_T$

13.  $R_{SC} = R_N = R_3 + \frac{R_1 \times R_2}{R_1 + R_2}$

14.  $I_L = \left[ \frac{R_N}{R_N + R_2} \right] I_N$

15.  $\phi = \frac{mmf}{S} = \frac{IN}{S}$

16.  $H = \frac{IN}{l}$

17.  $F = BlI$

18.  $E = Blv$

19.  $B = \frac{\phi}{a}$

20.  $E = \frac{\Delta\phi}{\Delta t} \cdot N$

21.  $E = \frac{L\Delta I}{\Delta t}$

22.  $L = \frac{\Delta\phi}{\Delta I} \cdot N$

23.  $Q = VC$

24.  $V = \frac{Q}{C}$

25.  $Q_{se} = Q_1 = Q_2 = Q_3 = \dots = Q_n$

26.  $Q_p = Q_1 + Q_2 + \dots + Q_n$

27.  $C_{se} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_n}}$

28.  $C_p = C_1 + C_2 + \dots + C_n$



**DIRECT CURRENT MACHINES**

**29.**  $E = \frac{2ZNp\phi}{60c}$

**30.**  $E = kN\phi$

**31.**  $c = 2a$

**32.**  $E = I_{sh}R_{sh} + L \frac{\Delta I}{\Delta t}$

**33.**  $R_{start} = \frac{(V - E)}{I_a} - R_a$

**34.**  $I_{a_{start}} = \frac{V}{R_a + R_{start}}$

**35.**  $E_{gen} = V + I_a R_a$

**36.**  $E_{mot} = V - I_a R_a$

**ALTERNATING CURRENT THEORY**

**37.**  $E_m = 2\pi BANn$

**38.**  $e = E_m \sin(2\pi f t + 1.57, 3)^0$

**39.**  $E_{rms} \text{ or } I_{rms} = 0,707 E_m \text{ or } I_m$

**40.**  $E_{ave} \text{ or } I_{ave} = 0,637 I_m \text{ or } I_m$

**41.**  $T = \frac{1}{f}$

**42.**  $f = \frac{Np}{60}$

**43.**  $\omega = 2\pi f$

**44.**  $Z = \sqrt{R^2 + X^2}$

**45.**  $\cos \phi = \frac{R}{Z}$

**46.**  $\tan \phi = \frac{X}{R}$

**47.**  $Z_L = R + j\omega L$

**48.**  $Z_C = R - j \frac{1}{\omega C}$

**49.**  $P = VI \cos \phi = I^2 R$

**50.**  $pf = \cos \phi = \frac{R}{Z}$

**51.**  $S = VI$

**52.**  $Q = VI \sin \phi$

**TRANSFORMERS**

**53.**  $E = 4,44 f \phi_m N$

**54.**  $k_t = \frac{N_1}{N_2} = \frac{V_1}{V_2} = \frac{E_1}{E_2} = \frac{I_2}{I_1}$

**ALTERNATING CURRENT MACHINES**

**55.**  $N_s = \frac{f}{p}$

**56.**  $s = \frac{N_s - N_r}{N_s}$



## MEASURING INSTRUMENTS

**57.**  $R_{sh} = \frac{I_m R_m}{I_{sh}}$

**58.**  $R_x = \frac{V}{I} - R_a$

**59.**  $R_{se} = \frac{V_t}{I_t} - R_m$

**60.**  $R_x = \frac{V}{I - I_v}$

## ALTERNATING CURRENT THEORY

$$V = E + IR$$

$$V = E_0 \cos(\omega t) + IR = IR + E_0 \cos(\omega t)$$

$$\frac{V}{E_0} = \frac{R}{R + jX} = \frac{R}{Z}$$

$$V = Z \cos(\omega t)$$

$$\frac{V}{E_0} = \frac{R}{R + jX} = \frac{R}{Z} = \frac{R}{\sqrt{R^2 + X^2}}$$

$$\frac{V}{E_0} = \frac{R}{R + jX} = \frac{R}{Z} = \frac{R}{\sqrt{R^2 + X^2}} = \frac{R}{\sqrt{R^2 + (\omega L)^2}}$$

$$\frac{V}{E_0} = \frac{R}{R + jX} = \frac{R}{Z} = \frac{R}{\sqrt{R^2 + X^2}} = \frac{R}{\sqrt{R^2 + (\omega L)^2}} = \frac{R}{\sqrt{R^2 + (\omega L)^2}}$$

$$Q = N A \mu_0$$

## TRANSFORMERS

$$\frac{V_1}{V_2} = \frac{N_1}{N_2} = \frac{I_2}{I_1}$$

## ALTERNATING CURRENT MACHINES

